



Calculator


Team Pi-Sense

Lochana Abhayawardana, Arsany Girgis and Emirkan Sali




Introduction

Block Diagram

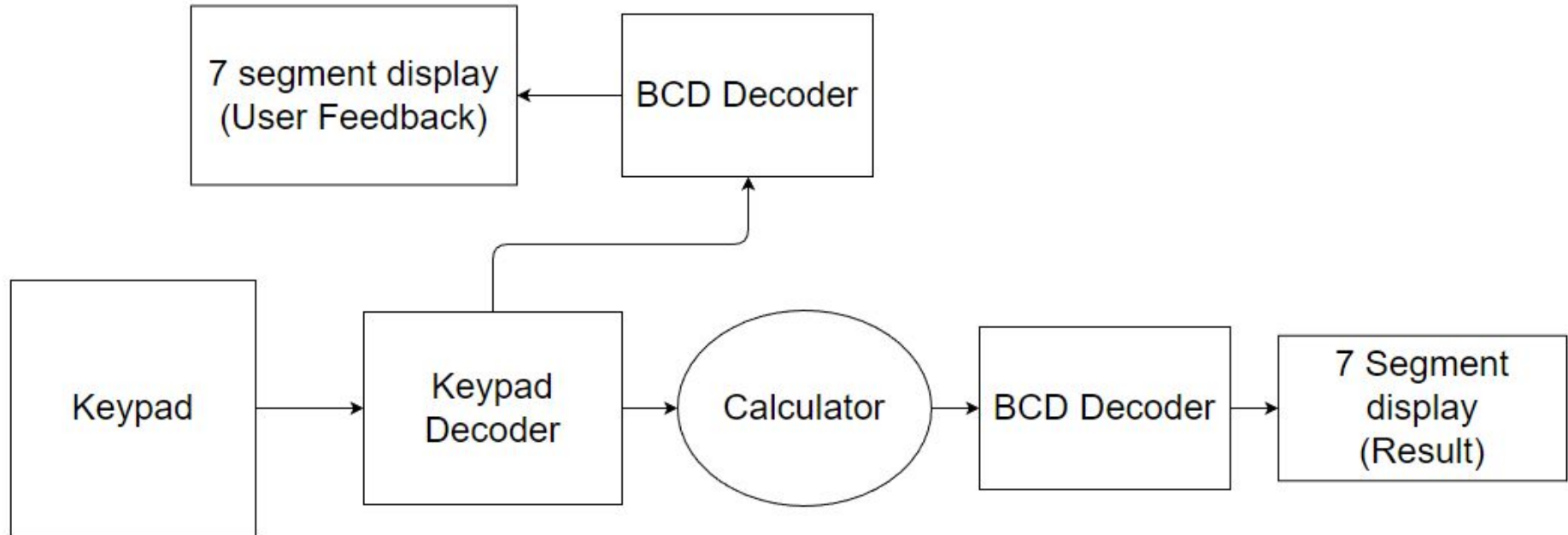

Sequence Diagram

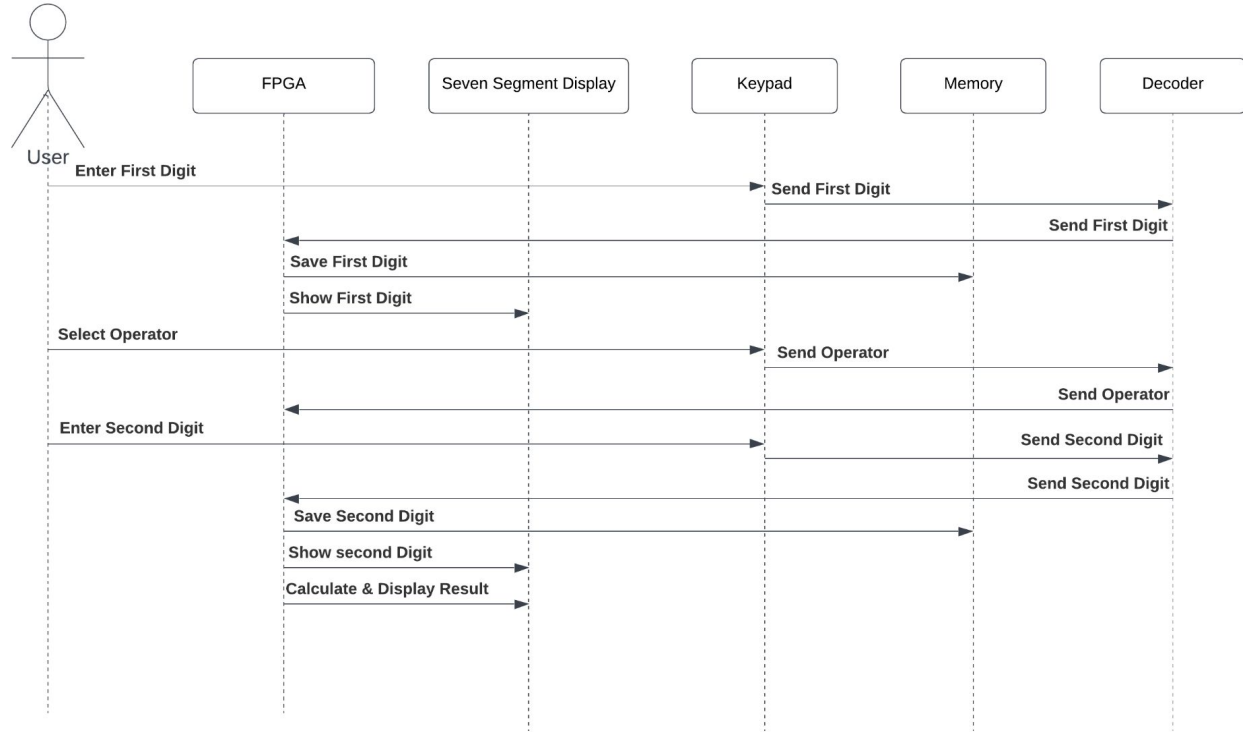



Implementation

Calculator



```
case op is
  when "00" => -- Addition operation
    temp(3 downto 0) := a_signed + b_signed;
    resultOut <= std_logic_vector(temp(3 downto 0));
    errorOut <= temp(4);
  when "01" => -- Subtraction operation
    temp(3 downto 0) := a_signed - b_signed;
    resultOut <= std_logic_vector(temp(3 downto 0));
    errorOut <= temp(4);
  when "10" => -- Multiplication operation
    temp := a_signed * b_signed;
    resultOut <= std_logic_vector(temp(3 downto 0));
    errorOut <= '0';

  when "11" => -- Division operation
    if b_signed /= 0 then
      quotient := a_signed / b_signed;
      remainder := a_signed rem b_signed;
      resultOut <= std_logic_vector(quotient(3 downto 0));
      errorOut <= remainder(0);

    else
      resultOut <= (others => 'X'); -- Indicate division by zero with 'X' output
      errorOut <= '1'; -- Set overflow to indicate an error condition
    end if;
  when others =>
    resultOut <= (others => 'X');
    errorOut <= 'X';
end case;
```

Decoder FSM



```
process (clk)
begin
    if rising_edge(clk) then
        if reset = '1' then
            prev_key <= "0000";
            key1_value <= "0000";
            key2_value <= "0000";
            key3_value <= "00";
            key1_assigned <= '0';
            key2_assigned <= '0';
            key3_assigned <= '0';
        else
            if DecodeOut /= prev_key then
                if key1_assigned = '0' then
                    key1_value <= DecodeOut;
                    key1_assigned <= '1';
                elsif key2_assigned = '0' then
                    key2_value <= DecodeOut;
                    key2_assigned <= '1';
                elsif key3_assigned = '0' then
                    key3_value <= DecodeOut(1 downto 0);
                    key3_assigned <= '1';
                end if;
            end if;
            prev_key <= DecodeOut;
        end if;
    end if;
end process;

Key1Assigned <= key1_assigned;
Key2Assigned <= key2_assigned;
Key3Assigned <= key3_assigned;
Key1Value <= key1_value;
Key2Value <= key2_value;
Key3Value <= key3_value;
```

Display

```
architecture Behavioral of DisplayController is
begin
    -- only display the leftmost digit
    anode<="1110";

    with DispVal select
        segOut <= "1000000" when "0000", --0
                  "1111001" when "0001", --1
                  "0100100" when "0010", --2
                  "0110000" when "0011", --3
                  "0011001" when "0100", --4
                  "0010010" when "0101", --5
                  "0000010" when "0110", --6
                  "1111000" when "0111", --7
                  "0000000" when "1000", --8
                  "0010000" when "1001", --9
                  "0001000" when "1010", --A
                  "0000011" when "1011", --B
                  "1000110" when "1100", --C
                  "0100001" when "1101", --D
                  "0000110" when "1110", --E
                  "0001110" when "1111", --F
                  "0111111" when others;

end Behavioral;
```

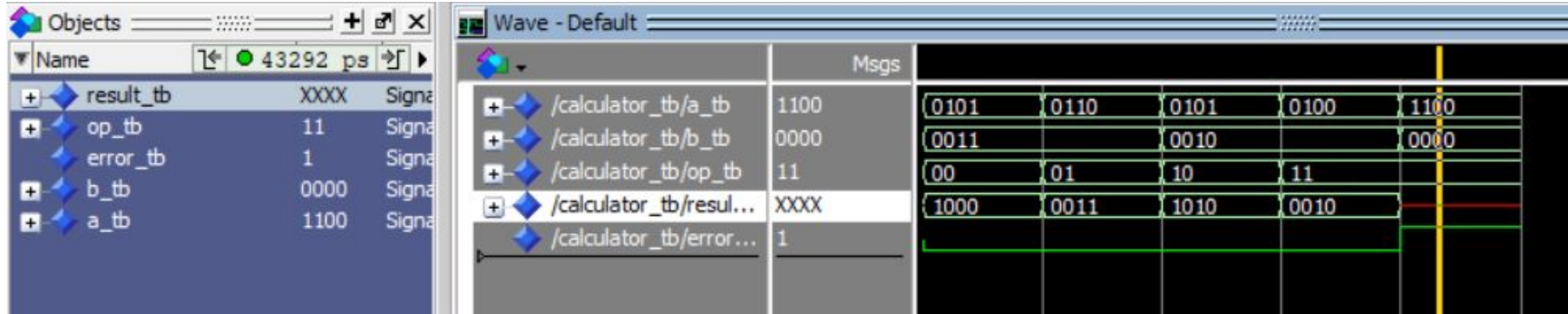

Top module




```
signal Decode: STD_LOGIC_VECTOR (3 downto 0);
signal result: STD_LOGIC_VECTOR (3 downto 0);
signal key1, key2: STD_LOGIC_VECTOR (3 downto 0);
signal key3: STD_LOGIC_VECTOR (1 downto 0);
begin

C0: Decoder port map (clk=>clk, Row =>JArow, Col=>JAcol, DecodeOut=> Decode);
C2: decoderFSM port map (clk=>clk, reset=>reset, DecodeOut => Decode, Key1Assigned =>LED1, Key2Assigned =>LED2, Key3Assigned =>LED3, Key1Value =>
C3: Calculator port map (a=>key1, b=>key2, op=>key3, resultOut=>result, errorOut=>LED4);
C4: DisplayController port map (DispVal=>result, anode=>an, segOut=>seg );
```

Calculator testbench



Decode FSM testbench

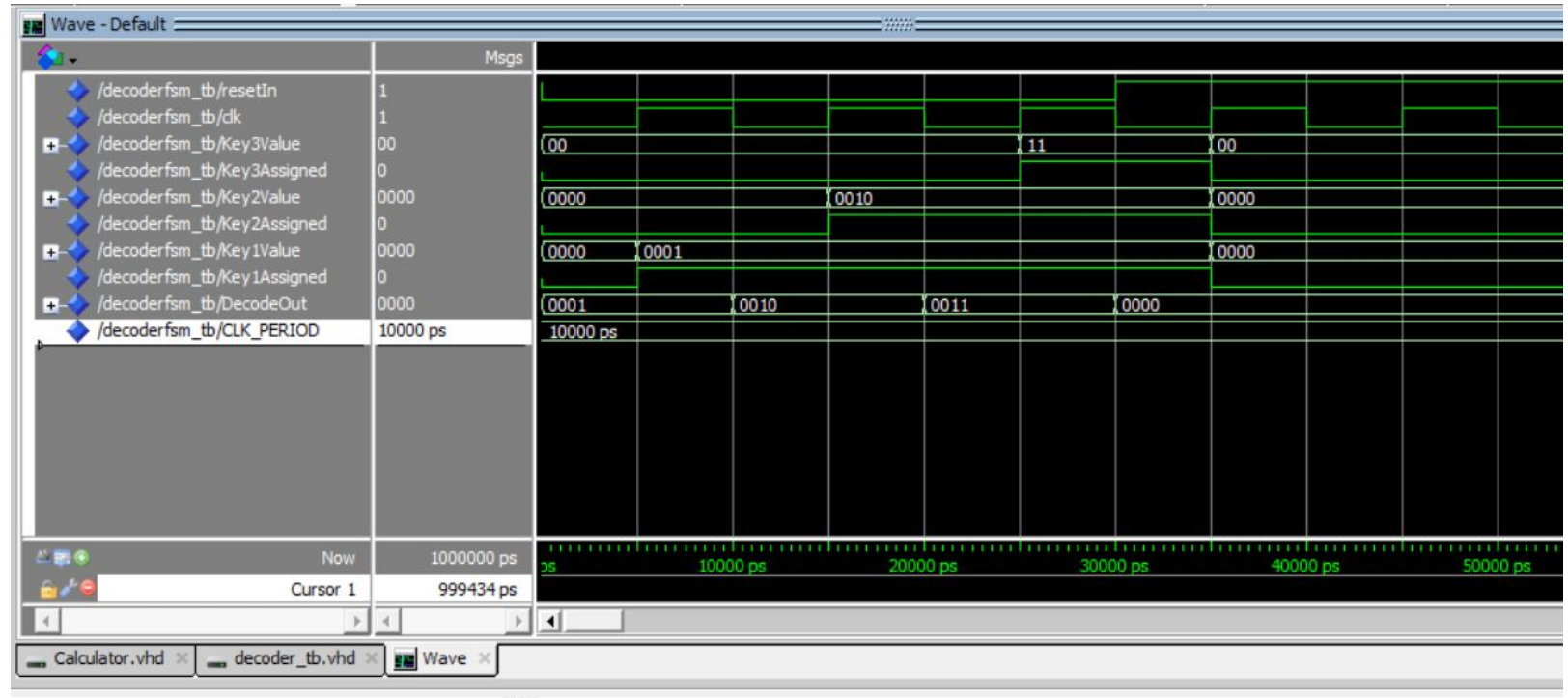





Schematic

Root page consisting of 5 subpages

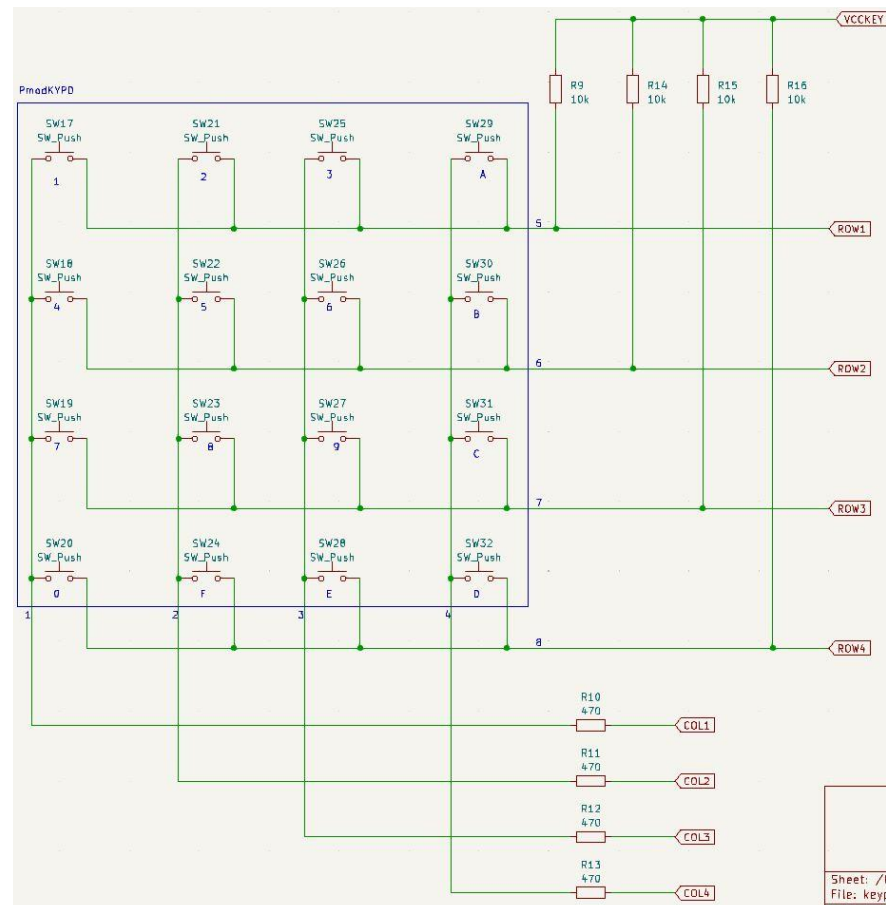1. Power page with Power supply, switch and LED
2. Keypad Page where we simulated the keypad using pushbuttons
3. FPGA page with the needed components of the FPGA
4. Seven segment display page with both displays
5. FPGA JTAG page for the JTAG Interface



Keypad using push-buttons

 


Seven Segment displays connected to the I/O ports of FPGA



PCB Design

 - Selecting the right footprints for the symbols
- Arranging the components in a way that makes sense
- Labeling, designing etc.
- Routing of connections using Autorouter





3D View of the PCB